

TASK-1 Design and Implementation of Digital Circuits in Verilog

VLSI Internship

Submitted By:

Sidhanth Krishnan



To the

Hardware Technology Group

Centre for Development of Advanced Computing

Centre In North East (CDAC-CINE)

Research Park, IIT Guwahati, Guwahati, Assam

June 2025

Contents

1	Design and Implementation of Digital Circuits in Verilog	1
1.1	1. Basic Logic Gates	1
1.2	2. Multiplexers	3
1.2.1	2:1 MUX	3
1.2.2	4:1 MUX	4
1.2.3	7:1 MUX	6
1.2.4	13:1 MUX	7
1.3	Binary to Gray and Gray to Binary Converters	9
1.4	Adders	11
1.4.1	Half Adder	11
1.4.2	Full Adder	12
1.4.3	Half Subtractor	13
1.4.4	Full Subtractor	14
1.5	4-bit Full Adder and Ripple Carry Adder	15
1.5.1	4-bit Full Adder Module	15
1.6	Priority Encoder	17
1.6.1	4:2 Priority Encoder	17
1.7	Latches	18
1.7.1	SR Latch	18
1.7.2	JK Latch	20
1.7.3	T Latch	21
1.7.4	D Latch	22
1.8	Flip-Flops	23
1.8.1	T Flip-Flop	23
1.8.2	SR Flip-Flop	24
1.8.3	JK Flip-Flop	26
1.8.4	D Flip-Flop	27
1.9	MOD 10 Counter	28
1.9.1	MOD 10 Asynchronous Counter	28
1.9.2	MOD 10 Synchronous Counter	30
1.10	Ring and Johnson Counters	31
1.10.1	4-bit Ring Counter	31
1.10.2	4-bit Johnson Counter	32
1.11	Universal Shift Register	34
1.12	Sequence Detectors for 10011 and 10101	35
1.12.1	1. Mealy Machine Sequence Detector for 10011 (Overlapping)	35
1.12.2	Mealy Machine Sequence Detector for 10011 (NON Overlapping)	37
1.12.3	Mealy Machine Sequence Detector for 10101 (Overlapping)	39
1.12.4	Mealy Machine Sequence Detector for 10101 (Non Overlapping)	40
1.12.5	Moore Machine Sequence Detector for 10101 (Overlapping)	41
1.12.6	Moore Machine Sequence Detector for 10101 (Non Overlapping)	42
1.13	Serial Moore and Mealy Adders	43

1 Design and Implementation of Digital Circuits in Verilog

This section details the implementation of digital logic circuits in Verilog across gate-level, dataflow, and behavioral modeling styles. All simulations were verified using waveform outputs.

1.1 1. Basic Logic Gates

 


Fig. 1: ALL Basic Logic Gates

Truth Table:

Table 1: AND Gate Truth Table

A	B	Y = A AND B
0	0	0
0	1	0
1	0	0
1	1	1

Table 2: OR Gate Truth Table

A	B	Y = A OR B
0	0	0
0	1	1
1	0	1
1	1	1

Table 3: NAND Gate Truth Table

A	B	Y = A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

Table 4: NOR Gate Truth Table

A	B	Y = A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

Table 5: XOR Gate Truth Table

A	B	Y = A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Table 6: XNOR Gate Truth Table

A	B	Y = A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

Table 7: NOT Gate Truth Table

A	Y = NOT A
0	1
1	0

Verilog Code Gate level:

```

module Logic_gates_Gatelevel(a,b,o1,o2,o3,o4,o5,o6,o7);
input a,b;
output o1,o2,o3,o4,o5,o6,o7;
and(o1,a,b);
or(o2,a,b);
nand(o3,a,b);
nor(o4,a,b);
xor(o5,a,b);
xnor(o6,a,b);
not(o7,a,b);
endmodule

```

Verilog Code Data flow:

```

module Logic_gates_Dataflow(a,b,o1,o2,o3,o4,o5,o6,o7,o8);
input a,b;
output o1,o2,o3,o4,o5,o6,o7,o8;
assign o1=a&&b;
assign o2=a||b;
assign o3=~(a&&b);
assign o4=~(a||b);
assign o5=a^b;

```

```

assign o6=~(a^b);
assign o7=~a;
assign o8=~b;
endmodule

```

Verilog Code Behavioral:

```

module Logic_gates_Behavioral(a,b,o1,o2,o3,o4,o5,o6,o7);
input a,b;
output o1,o2,o3,o4,o5,o6,o7;
reg o1,o2,o3,o4,o5,o6,o7;
always@(*) begin
o1=a&&b;
o2=a||b;
o3=~(a&&b);
o4=~(a||b);
o5=a^b;
o6=~(a^b);
o7=~a;
end
endmodule

```

1.2 2. Multiplexers

1.2.1 2:1 MUX

 


Fig. 2: 2:1 Multiplexer Circuit

Verilog Code 2x1 MUX:

```

module mux2x1(a,b,s,o);
input a,b,s;
output o;
assign o=(s==1)?b:a;
endmodule

module tb_mux2x1();
reg a, b, s;
wire o;

mux2x1 uut(.a(a), .b(b), .s(s), .o(o));

initial begin
$display("2:1 MUX Test");

```

```

$monitor("s=%b -> o=%b", s, o);
a = 0; b = 1; s = 0; #10;
s = 1; #10;
$finish;
end
endmodule

```

Table 8: 2:1 MUX Truth Table

S	I0	I1	Y
0	0	x	0
0	1	x	1
1	x	0	0
1	x	1	1

 


Fig. 3: 2:1 Multiplexer Circuit simulation

Simulation Observations

The 2:1 multiplexer was accurately realized

1.2.2 4:1 MUX

 


Fig. 4: 4:1 Multiplexer Circuit

Verilog Code 4x1 MUX:

```

module mux4x1(input [3:0] i,input [1:0] s,output o);
wire x1,x2;
mux2x1 m0(.a(i[0]),.b(i[1]),.s(s[0]),.o(x1));
mux2x1 m1(.a(i[2]),.b(i[3]),.s(s[0]),.o(x2));
mux2x1 m3(.a(x1),.b(x2),.s(s[1]),.o(o));
endmodule

module tb_mux4x1();
reg [3:0] i;
reg [1:0] s;
wire o;
mux4x1 uut(.i(i), .s(s), .o(o));
initial begin
i = 4'b1010;
s = 2'b00; #5; $display("s=%b -> o=%b", s, o);
s = 2'b01; #5; $display("s=%b -> o=%b", s, o);
s = 2'b10; #5; $display("s=%b -> o=%b", s, o);
s = 2'b11; #5; $display("s=%b -> o=%b", s, o);
$finish;
end
endmodule

```

Table 9: 4:1 MUX Truth Table

S1	S0	I0	I1	I2	I3	Y
0	0	x	x	x	x	I0
0	1	x	x	x	x	I1
1	0	x	x	x	x	I2
1	1	x	x	x	x	I3

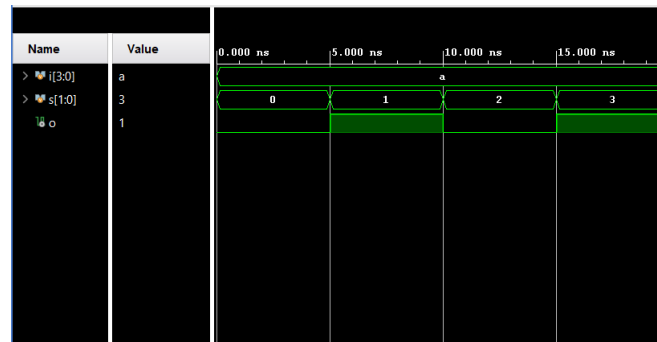


Fig. 5: 4:1 Multiplexer Circuit simulation

Simulation Observations

The 4:1 multiplexer was accurately realized

1.2.3 7:1 MUX

Table 10: 7:1 MUX Truth Table

S2	S1	S0	I0	I1	I2	I3	I4	I5	I6	Y
0	0	0	x	x	x	x	x	x	x	I0
0	0	1	x	x	x	x	x	x	x	I1
0	1	0	x	x	x	x	x	x	x	I2
0	1	1	x	x	x	x	x	x	x	I3
1	0	0	x	x	x	x	x	x	x	I4
1	0	1	x	x	x	x	x	x	x	I5
1	1	0	x	x	x	x	x	x	x	I6

Verilog Code 7x1 MUX:

```

module mux7x1(input [6:0] i, input [2:0] s, output o);
    wire [3:0] w1;
    wire [1:0] w2;
    wire dummy = 1'b0;
    mux2x1 m0 (.a(i[0]), .b(i[1]), .s(s[0]), .o(w1[0]));
    mux2x1 m1 (.a(i[2]), .b(i[3]), .s(s[0]), .o(w1[1]));
    mux2x1 m2 (.a(i[4]), .b(i[5]), .s(s[0]), .o(w1[2]));
    mux2x1 m3 (.a(i[6]), .b(dummy), .s(s[0]), .o(w1[3]));
    mux2x1 m4 (.a(w1[0]), .b(w1[1]), .s(s[1]), .o(w2[0]));
    mux2x1 m5 (.a(w1[2]), .b(w1[3]), .s(s[1]), .o(w2[1]));
    mux2x1 m6 (.a(w2[0]), .b(w2[1]), .s(s[2]), .o(o));
endmodule

module tb_mux7x1();
    reg [6:0] i;
    reg [2:0] s;
    wire o;

    mux7x1 uut(.i(i), .s(s), .o(o));

    initial begin
        $display("7:1 MUX Test");
        i = 7'b1010101;
        for (integer j = 0; j < 8; j = j + 1) begin
            s = j[2:0]; #5;
            $display("s=%b -> o=%b", s, o);
        end
        $finish;
    end
endmodule

```

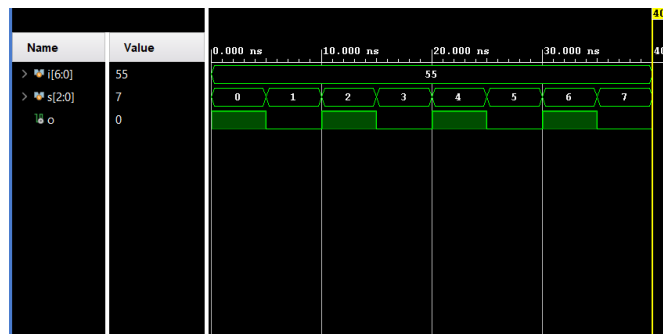


Fig. 6: 7:1 Multiplexer Circuit simulation

Simulation Observations

The 7:1 multiplexer was accurately realized

1.2.4 13:1 MUX

Table 11: 13:1 MUX Truth Table (Partial)

S3	S2	S1	S0	I0	I1	I2	I3	I4	I5	I6	I7	I8	I9	Y
0	0	0	0	x	x	x	x	x	x	x	x	x	x	I0
0	0	0	1	x	x	x	x	x	x	x	x	x	x	I1
0	0	1	0	x	x	x	x	x	x	x	x	x	x	I2
0	0	1	1	x	x	x	x	x	x	x	x	x	x	I3
0	1	0	0	x	x	x	x	x	x	x	x	x	x	I4
0	1	0	1	x	x	x	x	x	x	x	x	x	x	I5
0	1	1	0	x	x	x	x	x	x	x	x	x	x	I6
⋮	⋮	⋮	⋮						...					⋮
⋮	⋮													

Verilog Code 13x1 MUX:

```

module mux13x1(input [12:0] i, input [3:0] s, output o);
    wire [7:0] w1;
    wire [3:0] w2;
    wire [1:0] w3;
    wire dummy0 = 1'b0;
    wire dummy1 = 1'b0;
    wire dummy2 = 1'b0;

    mux2x1 m0 (.a(i[0]), .b(i[1]), .s(s[0]), .o(w1[0]));
    mux2x1 m1 (.a(i[2]), .b(i[3]), .s(s[0]), .o(w1[1]));
    mux2x1 m2 (.a(i[4]), .b(i[5]), .s(s[0]), .o(w1[2]));
    mux2x1 m3 (.a(i[6]), .b(i[7]), .s(s[0]), .o(w1[3]));
    mux2x1 m4 (.a(i[8]), .b(i[9]), .s(s[0]), .o(w1[4]));
    mux2x1 m5 (.a(i[10]), .b(i[11]), .s(s[0]), .o(w1[5]));
    mux2x1 m6 (.a(i[12]), .b(dummy0), .s(s[0]), .o(w1[6]));
    mux2x1 m7 (.a(dummy1), .b(dummy2), .s(s[0]), .o(w1[7]));

    mux2x1 m8 (.a(w1[0]), .b(w1[1]), .s(s[1]), .o(w2[0]));
    mux2x1 m9 (.a(w1[2]), .b(w1[3]), .s(s[1]), .o(w2[1]));
    mux2x1 m10 (.a(w1[4]), .b(w1[5]), .s(s[1]), .o(w2[2]));
    mux2x1 m11 (.a(w1[6]), .b(w1[7]), .s(s[1]), .o(w2[3]));

    mux2x1 m12 (.a(w2[0]), .b(w2[1]), .s(s[2]), .o(w3[0]));
    mux2x1 m13 (.a(w2[2]), .b(w2[3]), .s(s[2]), .o(w3[1]));

    mux2x1 m14 (.a(w3[0]), .b(w3[1]), .s(s[3]), .o(o));
endmodule

module tb_mux13x1;
    reg [12:0] i;
    reg [3:0] s;
    wire o;

    mux13x1 uut(.i(i), .s(s), .o(o));

    initial begin
        $display("13:1 MUX Test");
        i = 13'b1010011101110;
        for (integer k = 0; k < 16; k = k + 1) begin

```

```

        s = k[3:0]; #5;
        $display("s=%b -> o=%b", s, o);
    end
    $finish;
end
endmodule

```



Fig. 7: 13:1 Multiplexer Circuit simulation

Simulation Observations

The 13:1 multiplexer was accurately realized

1.3 Binary to Gray and Gray to Binary Converters

 


Fig. 8: Binary to Gray Code Converter

Verilog Code (Binary to Gray):

```

module BtoGrey(input [3:0]b,output reg [3:0]g);
reg prev;
integer i;
always@(*)begin
prev=1'b0;
for(i=3;i>=0;i=i-1)begin
g[i]=b[i]^prev;
prev=b[i];
end
end
endmodule
  
```

 


Fig. 9: Binary To Gray Code simulation

 


Fig. 10: Gray to Binary Code Converter

Verilog Code (Gray to Binary):

```
module GtoBinary(input [3:0] g,output reg [3:0] b);
reg prev;
integer i;
always@(*)begin
prev=1'b0;
for(i=3;i>=0;i=i-1)begin
b[i]=prev^g[i];
prev=b[i];
end
end
endmodule
```

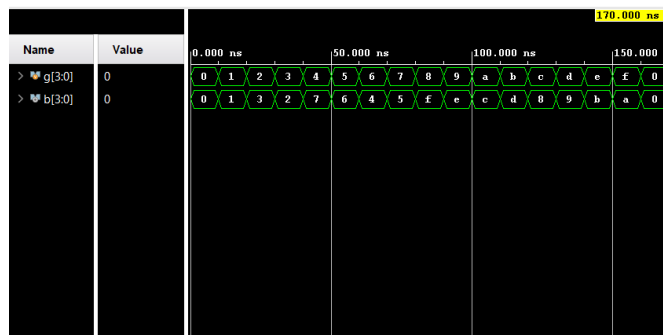


Fig. 11: Gray To Binary Code simulation

1.4 Adders

1.4.1 Half Adder

 


Fig. 12: Half Adder Circuit Diagram

Truth Table:

Table 12: Half Adder Truth Table

A	B	Sum (S), Carry (C)
0	0	0, 0
0	1	1, 0
1	0	1, 0
1	1	0, 1

Verilog Code:

```
module HA(a,b,s,c);  
input a,b;  
output s,c;  
assign s=a^b;  
assign c=a&b;  
endmodule
```

Testbench:

```
module tb_HA();  
reg a,b;  
wire s,c;  
HA uut(.a(a),.b(b),.s(s),.c(c));  
initial  
begin  
a=0; b=0;  
#10 a=0; b=1;  
#10 a=1; b=0;  
#10 a=1; b=1;  
#10 $finish;  
end  
endmodule
```

 


Fig. 13: Gray To Binary Code simulation

1.4.2 Full Adder

 


Fig. 14: Full Adder Circuit Diagram

Truth Table:

Table 13: Full Adder Truth Table

A	B	Cin	Sum (S), Cout
0	0	0	0, 0
0	0	1	1, 0
0	1	0	1, 0
0	1	1	0, 1
1	0	0	1, 0
1	0	1	0, 1
1	1	0	0, 1
1	1	1	1, 1

Verilog Code:

```
module FA(input a, input b, input cin, output s, output cout);
    assign s = a ^ b ^ cin;
    assign cout = (a & b) | (b & cin) | (a & cin);
endmodule
```

Testbench:

```
module tb_FA();
    reg [3:0] a;
    wire s,cout;
```

```

FA uut(.a(a[0]),.b(a[1]),.cin(a[2]),.s(s),.cout(cout));
initial begin
for(a=3'b000;a!=3'b111;a=a+3'b001)begin
#10;
end
#10;
$finish;
end
endmodule

```



Fig. 15: Gray To Binary Code simulation

1.4.3 Half Subtractor

 


Fig. 16: Half Subtractor Circuit Diagram

Truth Table:

Table 14: Half Subtractor Truth Table

A	B	Diff (D), Borrow (Bo)
0	0	0, 0
0	1	1, 1
1	0	1, 0
1	1	0, 0

Verilog Code:

```

module HS(a, b, d, b_out);
input a, b;
output d, b_out;

```

```

assign d = a ^ b;
assign b_out = ~a & b;
endmodule

```

Testbench:

```

module tb_HS();
  reg a, b;
  wire d, b_out;

  HS uut(.a(a), .b(b), .d(d), .b_out(b_out));

  initial begin
    a = 0; b = 0;
    #10 a = 0; b = 1;
    #10 a = 1; b = 0;
    #10 a = 1; b = 1;
    #10 $finish;
  end
endmodule
endmodule

```

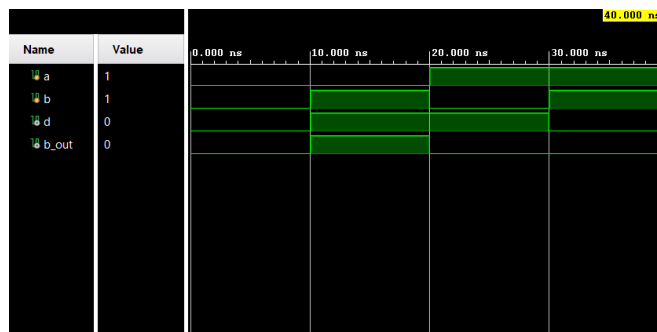


Fig. 17: Gray To Binary Code simulation

1.4.4 Full Subtractor

 


Fig. 18: Full Subtractor Circuit Diagram

Truth Table:

Table 15: Full Subtractor Truth Table

A	B	Bin	Diff (D), Bout
0	0	0	0, 0
0	0	1	1, 1
0	1	0	1, 1
0	1	1	0, 1
1	0	0	1, 0
1	0	1	0, 1
1	1	0	0, 0
1	1	1	1, 1

Verilog Code:

```
module FS(a, b, bin, d, bout);
    input a, b, bin;
    output d, bout;

    assign d = a ^ b ^ bin;
    assign bout = (~a & b) | ((~(a ^ b)) & bin);
endmodule
```

Testbench:

```
module tb_FS();
    reg [2:0] in;
    wire d, bout;

    FS uut(.a(in[0]), .b(in[1]), .bin(in[2]), .d(d), .bout(bout));
    integer i;
    initial begin
        for (i = 0; i < 8; i = i + 1) begin
            in = i[2:0];
            #10;
        end
        $finish;
    end
endmodule
```

 


Fig. 19: Full subtractor Simulation

1.5 4-bit Full Adder and Ripple Carry Adder

1.5.1 4-bit Full Adder Module

 


Fig. 20: 4-bit Full Adder Circuit

Verilog Code 4 bit adder:

```

module fourBIT_FA(input [3:0]a,input [3:0] b,input cin,output[3:0] o,output cout);
assign {cout,o}=a+b+cin;
endmodule

```

Verilog Code ripple adder:

```

module rippleadder(input [3:0]a,input [3:0] b,input cin,output[3:0] o,output cout);
wire c1,c2,c3;
FA f0(.a(a[0]),.b(b[0]),.cin(cin),.s(o[0]),.cout(c1));
FA f1(.a(a[1]),.b(b[1]),.cin(c1),.s(o[1]),.cout(c2));
FA f2(.a(a[2]),.b(b[2]),.cin(c2),.s(o[2]),.cout(c3));
FA f3(.a(a[3]),.b(b[3]),.cin(c3),.s(o[3]),.cout(cout));
endmodule

```

Table 16: 4-bit Ripple Carry Adder Sample Truth Table

A (4-bit)	B (4-bit)	Cin	Sum (4-bit)	Cout
0000	0000	0	0000	0
0101	0011	0	1000	0
1111	0001	0	0000	1
1010	0101	0	1111	0

Testbench for 4 bit adder:

```

module tb_fourBIT_FA();
reg [3:0]a;
reg [3:0]b;
reg cin;
wire [3:0]o;
wire cout;
fourBIT_FA uut (.a(a),.b(b),.cin(cin),.o(o),.cout(cout));
initial begin
a=4'b0000;
cin=0;
for(b=4'b0000;b<=4'b1111;b=b+4'b0001)begin
#10;
end
end
endmodule

```

 


Fig. 21: 4-bit Adder Simulation

Testbench for ripple adder:

```

module tb_rippleadder();
reg [3:0]a;
reg [3:0]b;
reg cin;
wire [3:0]o;
wire cout;

```

```

rippleadder uut (.a(a),.b(b),.cin(cin),.o(o),.cout(cout));
initial begin
a=4'b0000;
cin=0;
for(b=4'b0000;b<=4'b1111;b=b+4'b0001)begin
#10;
end
end
endmodule

```

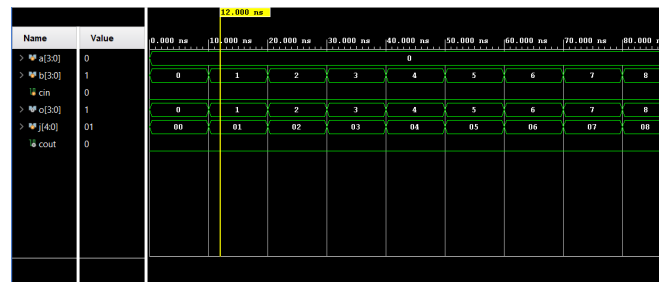


Fig. 22: ripple Adder Simulation

1.6 Priority Encoder

1.6.1 4:2 Priority Encoder

 


Fig. 23: 4:2 Priority Encoder Circuit

Verilog Code 4:2 Priority Encoder:

```

module priority_encoder(input [3:0] i,output [1:0] o);
assign o[1]=i[3]|i[2];
assign o[0]=i[3]|((~i[2])&i[1]);
endmodule

```

Table 17: 4:2 Priority Encoder Truth Table

I3	I2	I1	I0	O1	O0
0	0	0	1	0	0
0	0	1	x	0	1
0	1	x	x	1	0
1	x	x	x	1	1

Testbench:

```

module tb_priorityencoder();
reg [3:0] i;
wire [1:0] o;
priority_encoder uut(.i(i),.o(o));
initial
begin
i=4'b0000;
repeat(16)
begin
#10;
i=i+1;

end
$finish;

end
endmodule

```



Fig. 24: 4:2 Priority Encoder Simulation

1.7 Latches

1.7.1 SR Latch

 


Fig. 25: SR Latch Circuit

Verilog Code:

```

module SR_LATCH(input s,input r,input e,output reg q,output q_bar);
assign q_bar=!q;
always@(*)begin
if(e && (s|r))begin

```

```

        if(s && r) q=1'bx;
        else q=s;
    end

end

endmodule

```

Table 18: SR Latch Truth Table

S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Invalid	Invalid

Testbench:

```

module tb_SR_LATCH();
    reg s, r, e;
    wire q, q_bar;
    reg [3:0] vec;
    SR_LATCH uut (
        .s(s),
        .r(r),
        .e(e),
        .q(q),
        .q_bar(q_bar)
    );

    initial begin
        for (vec = 4'b0000; vec <= 4'b0111; vec = vec + 1) begin
            {e,s,r}=vec[2:0];
            #10;
        end
        $finish;
    end
endmodule

```



Fig. 26: SR Latch Simulation

1.7.2 JK Latch

 


Fig. 27: JK Latch Circuit

Verilog Code:

```
module JK_latch(input j,input k,input e,output reg q,output q_bar);
assign q_bar=~q;
always@(*)begin

if(e)begin

if({j,k}==2'b01) q=0;
if({j,k}==2'b10) q=1;
if({j,k}==2'b11) q=~q;

end

end
endmodule
```

Table 19: JK Latch Truth Table

J	K	EN	Q(next)
0	0	1	Q
0	1	1	0
1	0	1	1
1	1	1	Q


Testbench:

```
module tb_JK_latch();
reg j, k, e;
wire q, q_bar;
reg [3:0] vec;
JK_latch uut (
.j(j),
.k(k),
.e(e),
.q(q),
.q_bar(q_bar)
);
initial begin
for (vec = 4'b0000; vec <= 4'b0111; vec = vec + 1) begin
{e, j, k} = vec[2:0];
#10;
end
$finish;
end
endmodule
```



Fig. 28: JK Latch Simulation

1.7.3 T Latch

 

1.7.4 D Latch

 


Fig. 30: D Latch Circuit

Verilog Code:

```
module D_latch(input d,input e,output reg q,output q_bar);
assign q_bar=~q;
always@(*)begin

if(e)begin
q=d;
end

end
endmodule
```

Table 21: D Latch Truth Table

D	EN	Q(next)
0	1	0
1	1	1

Testbench:

```
module tb_D_latch();
reg d, e;
wire q, q_bar;
reg [2:0] vec;
D_latch uut (
.d(d),
.e(e),
.q(q),
.q_bar(q_bar)
);

initial begin
for (vec = 3'b000; vec <= 3'b011; vec = vec + 1) begin
{e,d}=vec[1:0];
#10;
end
$finish;
end
endmodule
```




Fig. 31: D Latch Simulation

1.8 Flip-Flops

1.8.1 T Flip-Flop

 


Fig. 32: T Flip-Flop Circuit

Verilog Code:

```
'timescale 1ns / 1ps
module T_ff(input t, input clk, input pr, input cr, output reg q, output q_bar);
    assign q_bar = ~q;

    always @(posedge clk or negedge pr or negedge cr) begin
        if (!cr)
            q <= 0;
        else if (!pr)
            q <= 1;
        else if (t)
            q <= ~q;
        end
    end
endmodule
```

Table 22: T Flip-Flop Truth Table

T	Q (next)	Description
0	Q	Hold
1	$\sim Q$	Toggle

Testbench:

```
'timescale 1ns / 1ps
module tb_T_ff();
    reg t, clk, pr, cr;
    wire q, q_bar;

    T_ff uut(.t(t), .clk(clk), .pr(pr), .cr(cr), .q(q), .q_bar(q_bar));

    initial begin
```

```

    clk = 0;
    t = 0;
    pr = 1; cr = 0; #2;
    cr = 1; #2;
    t = 1; #10;
    t = 0; #10;
    t = 1; #10;
    $finish;
end

always #5 clk = ~clk;
endmodule

```

 


Fig. 33: T Flip-Flop Simulation

1.8.2 SR Flip-Flop

 


Fig. 34: SR Flip-Flop Circuit

Verilog Code:

```

module SR_ff(input s,input r,input clk,output reg q,output q_bar);
assign q_bar=~q;
always@(posedge clk)begin
if({s,r}==2'b01) q<=0;
if({s,r}==2'b10) q<=1;
if({s,r}==2'b11) q<=1'bx;
end
endmodule

```

 


Fig. 35: SR Flip-Flop using a T-FlipFlop

Verilog Code:

```
module SR_using_T(input s,input clk,input r,input pr,input cr,output q,output q_bar);
T_ff t0(.t((s&q_bar)|(r&q)),.clk(clk),.pr(pr),.cr(cr),.q(q),.q_bar(q_bar));
endmodule
```

Table 23: SR Flip-Flop Truth Table

S	R	Q(next)	Description
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	X	Invalid

Testbench:

```
module tb_sr_ff();
reg clk;
reg s,r;
wire q,q_bar;
SR_ff uut(.clk(clk),.q(q),.s(s),.r(r),.q_bar(q_bar));
initial begin
clk=0;
s=0;r=0;
#10; s=0;r=1;
#10; s=1;r=0;
#10; s=0;r=0;
#10 $finish;
end

always begin
#5;
clk=~clk;
end

endmodule
```



Fig. 36: SR Flip-Flop Simulation

1.8.3 JK Flip-Flop

 


Fig. 37: JK Flip-Flop Circuit

Verilog Code:

```
module JK_ff(input j,input k,input clk,output reg q,output q_bar);
assign q_bar=~q;
always@(posedge clk)begin
if({j,k}==2'b01) q<=0;
if({j,k}==2'b10) q<=1;
if({j,k}==2'b11) q<=~q;
end
endmodule
```

 


Fig. 38: JK Flip-Flop using T-FlipFlop

Verilog Code:

```
module JK_using_T(input j,input k,input clk,input pr,input cr,output q,output q_bar);
wire t=(j & ~q) | (k & q);
T_ff t0(.t(t),.clk(clk),.pr(pr),.cr(cr),.q(q),.q_bar(q_bar));
endmodule
```

Table 24: JK Flip-Flop Truth Table

J	K	Q(next)	Description
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	$\sim Q$	Toggle

Testbench:

```
module tb_jk_ff();
reg clk;
reg j,k;
wire q,q_bar;
JK_ff uut(.clk(clk),.q(q),.j(j),.k(k),.q_bar(q_bar));
initial begin
clk=0;
end
```

```

j=0;k=0;
#10; j=0;k=1;
#10; j=1;k=0;
#10; j=0;k=0;
#10 $finish;
end

always begin
#5;
clk=~clk;
end

endmodule

```



Fig. 39: JK Flip-Flop Simulation

1.8.4 D Flip-Flop

 


Fig. 40: D Flip-Flop Circuit

Verilog Code:

```

module D_ff(input d,output q,output q_bar,input clk);
SR_ff m0(.s(d),.r(~d),.q(q),.q_bar(q_bar),.clk(clk));
endmodule

```

 


Fig. 41: D Flip-Flop Circuit

Verilog Code:

```

module D_using_T(input d,input clk,input pr,input cr,output q,output q_bar);
wire t=d~q;
T_ff t0(.t(t),.clk(clk),.pr(pr),.cr(cr),.q(q),.q_bar(q_bar));
endmodule

```

Table 25: D Flip-Flop Truth Table

D	Q(next)	Description
0	0	Reset
1	1	Set

Testbench:

```

module tb_d_ff();
  reg clk, d;
  wire q, q_bar;
  D_ff uut(.d(d), .clk(clk), .q(q), .q_bar(q_bar));
  initial begin
    clk=0;
    d = 0; #10;
    d = 1; #10;
    d = 0; #10;
    d = 1; #10;
    $finish;
  end
  always #5 clk = ~clk;
endmodule

```

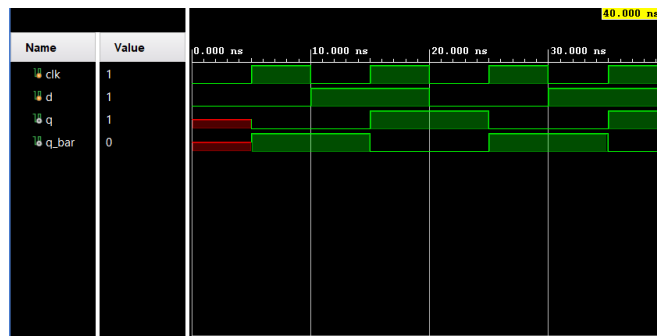


Fig. 42: D Flip-Flop Simulation

1.9 MOD 10 Counter

1.9.1 MOD 10 Asynchronous Counter

 


Fig. 43: MOD-10 Asynchronous Counter Circuit

Verilog Code:

```

`timescale 1ns / 1ps

```

```

module T_ff1(input t, input clk, input pr, input cr, output reg q, output q_bar);
    assign q_bar = ~q;

    always @(negedge clk or negedge pr or negedge cr) begin
        if (!cr)
            q = 0;
        else if (!pr)
            q = 1;
        else if (t)
            q <= ~q;
        end
    endmodule

module mod10_async_counter(input clk1, input r, output [3:0] count);
    wire [3:0] q;
    wire internal_reset;

    // Active-low reset (0 when q == 10)
    assign internal_reset = ~(q == 4'd10); // 0 when we want to clear

    wire cr = r & internal_reset; // final cr input to T_ff1

    T_ff1 t0(.t(1), .clk(clk1), .pr(1), .cr(cr), .q(q[0]), .q_bar());
    T_ff1 t1(.t(1), .clk(q[0]), .pr(1), .cr(cr), .q(q[1]), .q_bar());
    T_ff1 t2(.t(1), .clk(q[1]), .pr(1), .cr(cr), .q(q[2]), .q_bar());
    T_ff1 t3(.t(1), .clk(q[2]), .pr(1), .cr(cr), .q(q[3]), .q_bar());

    assign count = q;
endmodule

```

Table 26: MOD-10 Asynchronous Counter Sequence

Clock Pulse	Count Output (Decimal)
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	0

Testbench:

```

`timescale 1ns / 1ps
module tb_mod10_async_counter();
    reg clk;
    reg r;
    wire [3:0] count;

    mod10_async_counter uut(.clk1(clk), .r(r), .count(count));

    initial begin
        clk = 0;
        r = 0; #5;
        r = 1;
        #200;
        $finish;
    end

    always #5 clk = ~clk;
endmodule

```

```
endmodule
```

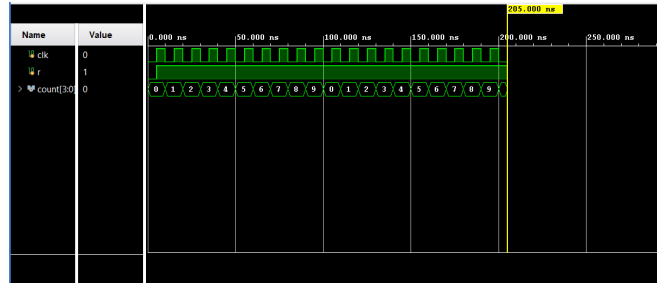


Fig. 44: MOD-10 Asynchronous Counter Simulation

1.9.2 MOD 10 Synchronous Counter

 


Fig. 45: MOD-10 Synchronous Counter Circuit

Verilog Code:

```
'timescale 1ns / 1ps

// 9. Mod-10 Synchronous Up-Counter
module mod10_sync_counter(input clk, input reset, output reg [3:0] count);
    always @(posedge clk or posedge reset) begin
        if (reset) count <= 0;
        else if (count == 9) count <= 0;
        else count <= count + 1;
    end
endmodule
```

Table 27: MOD-10 Synchronous Counter Sequence

Clock Pulse	Count Output (Decimal)
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	0

Testbench:


```

`timescale 1ns / 1ps
module tb_mod10_sync_counter();
    reg clk, reset;
    wire [3:0] count;
    mod10_sync_counter uut(.clk(clk), .reset(reset), .count(count));
    initial begin
        clk = 0; reset = 1; #5;
        reset = 0; #100;
        $finish;
    end
    always #5 clk = ~clk;
endmodule

```

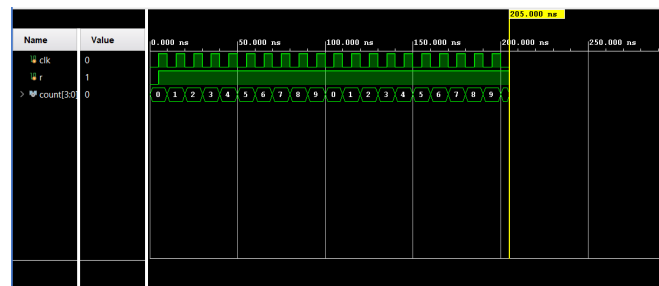


Fig. 46: MOD-10 Synchronous Counter Simulation

1.10 Ring and Johnson Counters

1.10.1 4-bit Ring Counter

 


Fig. 47: 4-bit Ring Counter Circuit

Verilog Code:

```

`timescale 1ns / 1ps
module ring_counter(input clk, input reset, output reg [3:0] out);
    always @(posedge clk or posedge reset) begin
        if (reset) out <= 4'b0001;
        else out <= {out[2:0], out[3]};
    end
endmodule

```

Table 28: 4-bit Ring Counter Sequence

Clock Pulse	Output (Binary)
0	1000
1	0001
2	0010
3	0100
4	1000
5	0001

Testbench:

```
'timescale 1ns / 1ps
module tb_ring_counter();
  reg clk, reset;
  wire [3:0] out;
  ring_counter uut(.clk(clk), .reset(reset), .out(out));
  initial begin
    clk = 0; reset = 1; #5;
    reset = 0; #100;
    $finish;
  end
  always #5 clk = ~clk;
endmodule
```

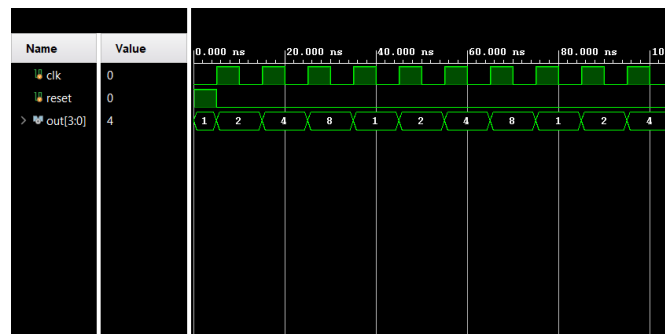


Fig. 48: 4-bit Ring Counter Simulation

1.10.2 4-bit Johnson Counter

 


Fig. 49: 4-bit Johnson Counter Circuit

Verilog Code:

```
'timescale 1ns / 1ps
module johnson_counter(input clk, input reset, output reg [3:0] out);
  always @(posedge clk or posedge reset) begin
    if (reset) out <= 4'b0000;
  end
endmodule
```

```

    else out <= {~out[0], out[3:1]};
end
endmodule

```

Table 29: 4-bit Johnson Counter Sequence

Clock Pulse	Output (Binary)
0	0000
1	1000
2	1100
3	1110
4	1111
5	0111
6	0011
7	0001
8	0000

Testbench:

```

`timescale 1ns / 1ps
module tb_johnson_counter();
    reg clk, reset;
    wire [3:0] out;
    johnson_counter uut(.clk(clk), .reset(reset), .out(out));
    initial begin
        clk = 0; reset = 1; #5;
        reset = 0; #100;
        $finish;
    end
    always #5 clk = ~clk;
endmodule

```

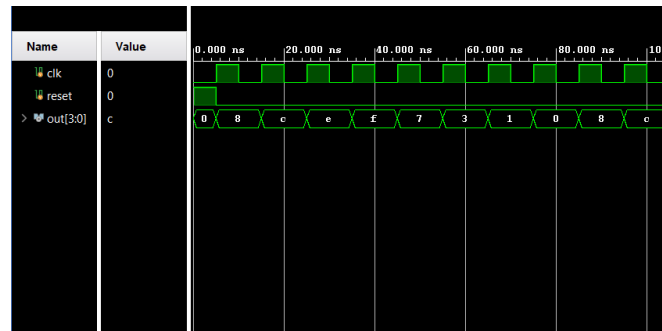


Fig. 50: 4-bit Johnson Counter Simulation

1.11 Universal Shift Register

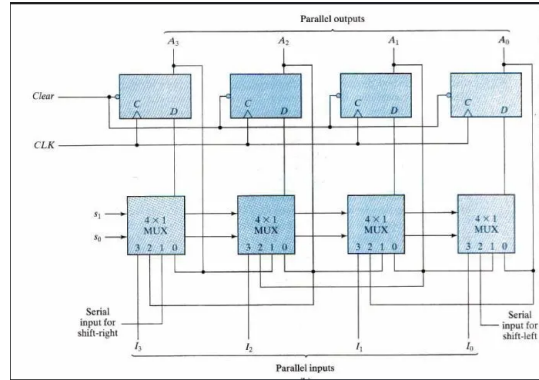


Fig. 51: 4-bit Universal Shift Register Circuit

Verilog Code:

```
'timescale 1ns / 1ps
module universal_shift_register(input [1:0] sel, input [3:0] d, input clk, input reset, output reg [3:0]
    q);
    always @(posedge clk or posedge reset) begin
        if (reset) q <= 0;
        else case (sel)
            2'b00: q <= q;
            2'b01: q <= {q[2:0], d[0]};
            2'b10: q <= {d[3], q[3:1]};
            2'b11: q <= d;
        endcase
    end
endmodule
```

Table 30: Universal Shift Register Operations

Select	Operation	Description	Example (q = 1010)
00	Hold	No change	1010
01	Shift Right	q = S _{in_R} , q ₃ , q ₂ , q ₁	e.g., S _{in_R} = 1 → 1101
10	Shift Left	q = q ₂ , q ₁ , q ₀ , S _{in_L}	e.g., S _{in_L} = 0 → 0100
11	Parallel Load	q = Parallel Input	e.g., P _{in} = 1111 → 1111

Testbench:

```
'timescale 1ns / 1ps
module tb_universal_shift_register();
    reg [1:0] sel;
    reg [3:0] d;
    reg clk, reset;
    wire [3:0] q;
    universal_shift_register uut(.sel(sel), .d(d), .clk(clk), .reset(reset), .q(q));
    initial begin
        clk = 0; reset = 1; #5;
        reset = 0; sel = 2'b11; d = 4'b1010; #10;
        sel = 2'b01; d = 4'b0001; #10;
        sel = 2'b10; #10;
        sel = 2'b00; #10;
        $finish;
    end
    always #5 clk = ~clk;
endmodule
```



Fig. 52: 4-bit Universal Shift Register Simulation

1.12 Sequence Detectors for 10011 and 10101

1.12.1 1. Mealy Machine Sequence Detector for 10011 (Overlapping)

 


Fig. 53: Mealy FSM for sequence 10011 (Overlapping)

Verilog Code:

```

module mealy_10011_ov(input clk, input rst, input in, output reg out);
  reg [2:0] state, next;
  parameter S0=0, S1=1, S2=2, S3=3, S4=4;
  always @(posedge clk or posedge rst) begin
    if (rst) state <= S0;
    else state <= next;
  end
  always @(*) begin
    out = 0;
    case (state)
      S0: next = in ? S1 : S0;
      S1: next = in ? S1 : S2;
      S2: next = in ? S3 : S0;
      S3: next = in ? S1 : S4;
      S4: begin next = in ? S1 : S0; out = in; end
    endcase
  end
endmodule

```

2. Moore Machine Sequence Detector for 10011 (Overlapping)

 


Fig. 54: Moore FSM for sequence 10011 (Overlapping)

Verilog Code:

```

`timescale 1ns / 1ps
module moore_10011_ov(input clk, input rst, input in, output reg out);
    reg [2:0] state, next;
    parameter S0=0, S1=1, S2=2, S3=3, S4=4, S5=5;
    always @(posedge clk or posedge rst) begin
        if (rst) state <= S0;
        else state <= next;
    end
    always @(*) begin
        case (state)
            S0: next = in ? S1 : S0;
            S1: next = in ? S1 : S2;
            S2: next = in ? S3 : S0;
            S3: next = in ? S1 : S4;
            S4: next = in ? S5 : S0;
            S5: next = in ? S1 : S0;
        endcase
    end
    always @(*) begin
        out = (state == S5);
    end
endmodule

```

1.12.2 Mealy Machine Sequence Detector for 10011 (NON Overlapping)

 


Fig. 55: Mealy FSM for sequence 10011 (Non Overlapping)

Verilog Code:

```

module mealy_10011_nov(input clk, input rst, input in, output reg out);
  reg [2:0] state, next;
  parameter S0=0, S1=1, S2=2, S3=3, S4=4;
  always @(posedge clk or posedge rst) begin
    if (rst) state <= S0;
    else state <= next;
  end
  always @(*) begin
    out = 0;
    case (state)
      S0: next = in ? S1 : S0;
      S1: next = in ? S1 : S2;
      S2: next = in ? S3 : S0;
      S3: next = in ? S1 : S4;
      S4: begin next = in ? S0 : S0; out = in; end
    endcase
  end
end
endmodule

```

Moore Machine Sequence Detector for 10011 (NON Overlapping)

 


Fig. 56: Moore FSM for sequence 10011 (Non Overlapping)

Verilog Code:

```

module moore_10011_nov(input clk, input rst, input in, output reg out);
  reg [2:0] state, next;
  parameter S0=0, S1=1, S2=2, S3=3, S4=4, S5=5;
  always @(posedge clk or posedge rst) begin
    if (rst) state <= S0;
    else state <= next;
  end
  always @(*) begin
    case (state)
      S0: next = in ? S1 : S0;
      S1: next = in ? S1 : S2;
      S2: next = in ? S3 : S0;
      S3: next = in ? S1 : S4;
      S4: next = in ? S5 : S0;
      S5: next = in ? S0 : S0;
    endcase
  end
  always @(*) begin
    out = (state == S5);
  end
endmodule

```


1.12.3 Mealy Machine Sequence Detector for 10101 (Overlapping)

 


Fig. 57: Mealy FSM for sequence 10101 (Overlapping)

Verilog Code:

```

module mealy_10101_ov(input clk, input rst, input in, output reg out);
    reg [2:0] state;
    parameter S0=0, S1=1, S2=2, S3=3, S4=4;

    always @(posedge clk or posedge rst) begin
        if (rst)
            state <= S0;
        else begin
            case (state)
                S0: state <= (in) ? S1 : S0;
                S1: state <= (in) ? S1 : S2;
                S2: state <= (in) ? S3 : S0;
                S3: state <= (in) ? S1 : S4;
                S4: state <= (in) ? S1 : S0;
            endcase
        end
    end

    always @(*) begin
        case (state)
            S4: out = (in) ? 1 : 0;
            default: out = 0;
        endcase
    end
endmodule

```

1.12.4 Mealy Machine Sequence Detector for 10101 (Non Overlapping)

 


Fig. 58: Mealy FSM for sequence 10101 (Non overlapping)

Verilog Code:

```

module mealy_10101_nov(input clk, input rst, input in, output reg out);
  reg [2:0] state, next;
  parameter S0=0, S1=1, S2=2, S3=3, S4=4;
  always @(posedge clk or posedge rst) begin
    if (rst) state <= S0;
    else state <= next;
  end
  always @(*) begin
    out = 0;
    case (state)
      S0: next = in ? S1 : S0;
      S1: next = in ? S1 : S2;
      S2: next = in ? S3 : S0;
      S3: next = in ? S4 : S2;
      S4: begin next = in ? S0 : S0; out = ~in; end
    endcase
  end
end
endmodule
endmodule

```

1.12.5 Moore Machine Sequence Detector for 10101 (Overlapping)

 


Fig. 59: Moore FSM for sequence 10101 (Overlapping)

Verilog Code:

```
'timescale 1ns / 1ps
module moore_10101_ov(input clk, input rst, input in, output reg out);
    reg [2:0] state, next;
    parameter S0=0, S1=1, S2=2, S3=3, S4=4, S5=5;
    always @(posedge clk or posedge rst) begin
        if (rst) state <= S0;
        else state <= next;
    end
    always @(*) begin
        case (state)
            S0: next = in ? S1 : S0;
            S1: next = in ? S1 : S2;
            S2: next = in ? S3 : S0;
            S3: next = in ? S4 : S2;
            S4: next = in ? S5 : S0;
            S5: next = in ? S1 : S0;
        endcase
    end
    always @(*) begin
        out = (state == S5);
    end
endmodule
```

1.12.6 Moore Machine Sequence Detector for 10101 (Non Overlapping)

 


Fig. 60: Moore FSM for sequence 10101 (Non Overlapping)

Verilog Code:

```

`timescale 1ns / 1ps
module moore_10101_nov(
    input clk,
    input reset,
    input in,
    output reg out
);

typedef enum reg [2:0] {
    S0, S1, S2, S3, S4, S5
} state_t;

state_t state, next_state;

always @(posedge clk or posedge reset) begin
    if (reset)
        state <= S0;
    else
        state <= next_state;
end

always @(*) begin
    case (state)
        S0: next_state = (in == 1) ? S1 : S0;
        S1: next_state = (in == 0) ? S2 : S1;
        S2: next_state = (in == 1) ? S3 : S0;
        S3: next_state = (in == 0) ? S4 : S1;
        S4: next_state = (in == 1) ? S5 : S0;
        S5: next_state = (in == 1) ? S1 : S0;
        default: next_state = S0;
    endcase
end

always @(*) begin
    out = (state == S5) ? 1 : 0;
end
endmodule

```

1.13 Serial Moore and Mealy Adders

Moore Machine Serial Adder

 


Fig. 61: Serial Adder using Moore Machine

 


Fig. 62: Serial Adder using Moore Machine

Verilog Code:

```
'timescale 1ns / 1ps
module serial_adder_moore(
    input clk, rst, a_bit, b_bit,
    output reg sum, carry_out
);
    reg carry;

    always @(posedge clk or posedge rst) begin
        if (rst) begin
            carry <= 0;
            sum <= 0;
        end else begin
            sum <= a_bit ^ b_bit ^ carry;
            carry <= (a_bit & b_bit) | (a_bit & carry) | (b_bit & carry);
        end
    end

    always @(posedge clk)
        carry_out <= carry;
endmodule
```

Table 31: Moore Serial Adder Operation

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Testbench:

```

`timescale 1ns / 1ps
module tb_serial_adder_moore();

    reg clk, rst, a_bit, b_bit;
    wire sum, carry_out;

    serial_adder_moore uut(
        .clk(clk),
        .rst(rst),
        .a_bit(a_bit),
        .b_bit(b_bit),
        .sum(sum),
        .carry_out(carry_out)
    );

    // Clock generation
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    // Stimulus
    initial begin
        rst = 1; #10;
        rst = 0;

        // Test input bits: A = 1011, B = 1101 (LSB first)
        a_bit = 1; b_bit = 1; #10;
        a_bit = 1; b_bit = 0; #10;
        a_bit = 0; b_bit = 1; #10;
        a_bit = 1; b_bit = 1; #10;

        $finish;
    end
endmodule

```



Fig. 63: Moore Serial Adder Simulation

Mealy Machine Serial Adder

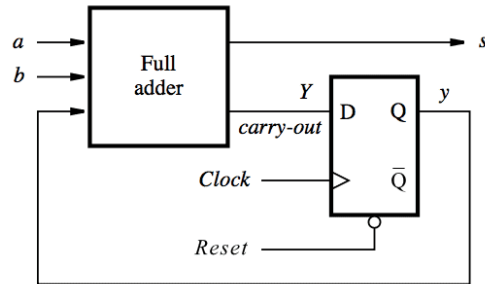


Fig. 64: Serial Adder using Mealy Machine

 


Fig. 65: Serial Adder using Mealy Machine

Verilog Code:

```
'timescale 1ns / 1ps
module serial_adder_mealy(
    input clk, rst, a_bit, b_bit,
    output reg sum, carry_out
);
    reg carry;

    always @(posedge clk or posedge rst) begin
        if (rst)
            carry <= 0;
        else begin
            sum <= a_bit ^ b_bit ^ carry;
            carry <= (a_bit & b_bit) | (a_bit & carry) | (b_bit & carry);
        end
    end

    always @(*) begin
        carry_out = carry;
    end
endmodule
```

Table 32: Mealy Serial Adder Operation

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Testbench:

```

`timescale 1ns / 1ps
module tb_serial_adder_mealy();

    reg clk, rst, a_bit, b_bit;
    wire sum, carry_out;

    serial_adder_mealy uut(
        .clk(clk),
        .rst(rst),
        .a_bit(a_bit),
        .b_bit(b_bit),
        .sum(sum),
        .carry_out(carry_out)
    );

    // Clock generation
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    // Stimulus
    initial begin
        rst = 1; #10;
        rst = 0;

        // Test input bits: A = 1011, B = 1101 (LSB first)
        a_bit = 1; b_bit = 1; #10;
        a_bit = 1; b_bit = 0; #10;
        a_bit = 0; b_bit = 1; #10;
        a_bit = 1; b_bit = 1; #10;

        $finish;
    end
endmodule

```

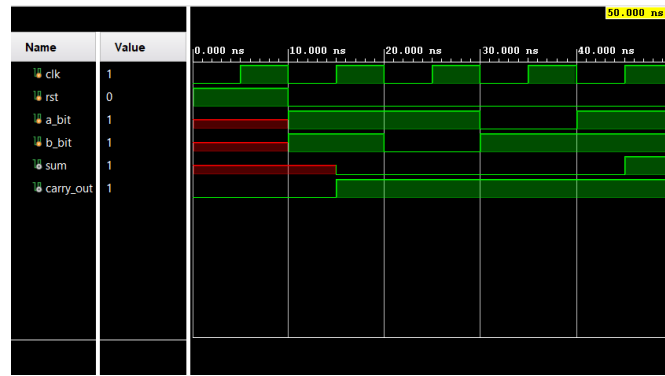



Fig. 66: Mealy Serial Adder Simulation